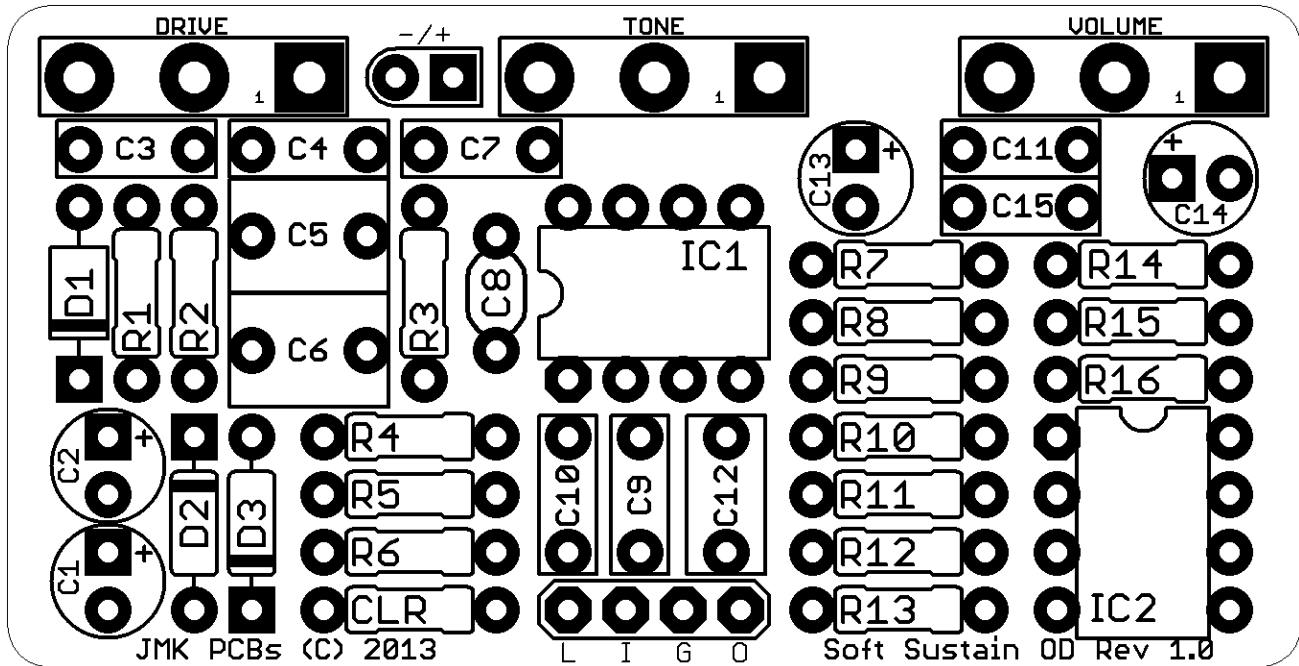


JMK PCBs PRESENTS...

# SOFT SUSTAIN DRIVE

PCB AND SCHEMATIC ARTWORK (C) 2014 JMK PEDALS

VERSION 1.0.1: 03/10/2014



| Resistors |      |     |      | Capacitors |       |     |       | Semiconductors       |          |
|-----------|------|-----|------|------------|-------|-----|-------|----------------------|----------|
| R1        | 510R | R10 | 1M   | C1         | 10uF  | C9  | 10nF  | IC1                  | LM741    |
| R2        | 10K  | R11 | 10K  | C2         | 100uF | C10 | 1nF   | IC2                  | TL071    |
| R3        | 150K | R12 | 10K  | C3         | 4.7nF | C11 | 10nF  | <b>Diodes</b>        |          |
| R4        | 1M   | R13 | 1M   | C4         | 10nF  | C12 | 220nF | D1                   | 1N4001   |
| R5        | 150K | R14 | 100R | C5         | 1uF   | C13 | 10uF  | D2, D3               | Clipping |
| R6        | 180K | R15 | 10K  | C6         | 470nF | C14 | 22uF  | <b>Potentiometer</b> |          |
| R7        | 100K | R16 | 6.8K | C7         | 10nF  | C15 | 1nF   | GAIN                 | B50K     |
| R8        | 2.4K | CLR | 4.7K | C8         | 10pF  |     |       | TONE                 | W20K     |
| R9        | 1M   |     |      |            |       |     |       | LEVEL                | A10K     |

This Document is designed for personal use only! Do not use this to create a product for sale without permission of it's owner: [jmkpcbs@gmail.com](mailto:jmkpcbs@gmail.com)



# BUILD NOTES

- The Soft Sustain OD is a near clone of a popular european builder's overdrive circuit, the SS-2. It features a pair of single op amps, so you can mix your gain stage and makeup stage op amps, for instance, using a lower fidelity op amp in the gain stage (LM741) with a fairly clean higher fidelity op amp in the makeup stage (TL071). It also features hard clipping with a parallel capacitor after the gain stage to generate clipping.
- Lots of fun can be had with this circuit, with lots of experimentation available with the tone section, the gain section, the clipping, and makeup stages being fairly flexible. Feel free to experiment with any elements that you might want to tweak!
- Hooking up the PCB is pretty simple, but to clarify: L = the connection for the + end of an LED; I = PCB Input; G = Ground for the Switch; O = PCB Output; + = 9V input; - = Ground for DC Jack; GND = Extra Ground for 1/4" Jack
- The ICs used in this project are very influential on the tone and character of the drive. Keep in mind that the pinout of the IC needs to be considered when installing, but otherwise, every single op amp IC you can think of is an option here.. **We highly recommend socketing your IC!** Options to try include, but is not limited to: LM741, LM 351, CA3140/30, TL061, TL071, NE5534 and LM386.

# TRUE BYPASS WIRING DIAGRAM

